 


## Logic Circuit Styles

Ken Stevens

## Logic Circuit Styles

- Two main aspects determine quality of design
  - Architecture
  - Circuits



"Wine Goblet"

## Logic Circuit Styles

- Topology is a major factor in the quality of circuits
- Major freedom and creativity of CMOS canvas
- How to use topology to meet design goals is critical
- For example
  - Sample action potentials in cat's brain
  - Test and regulate temperature of exhaust from manifold
  - Sample and store optical wavelengths for video/image capture
  - ...

## Design Point

- Choose topology that best meets design targets
- Primary metrics may be:
  - Performance
  - Power
- Secondary metrics may be:
  - cost
  - robustness
  - testability
  - TTM (Time To Market/Money)
  - Area
  - Gain
  - ...

## Logic Choice

- Logic family should be based on:
  - Knowledge of circuit alternatives and characteristics
  - Matching of design requirements to circuit topology (both FET and interconnect)
  - Interfacing issues (timing, voltage, etc.)
  - CAD support: HLD, design, synthesis, ATPG, Formal Verification, ...
  - Products requirements: performance, power, area, reliability, TTM, ...

## General Logic Families

- Two orthogonal "classes"
- Logic Style
  - Static logic
  - Dynamic logic
- Functional Style
  - Combinational
  - Sequential

	static	dynamic
combinational		
sequential		

## Static Logic

- The standard logic
- Complementary *on-set* and *off-set* logic
- Boolean function representation
- Transitions not explicitly specified or optimized
  - ♦ Example:  $o = \overline{a + b}$ 
    - on-set:  $\{\overline{ab}\}$
    - off-set:  $\neg\text{on-set} = \{a, b\}$

## Dynamic Logic

- *Transition* logic
- Specifies *set* and *reset* transitions
- Static states not explicitly specified or optimized
- Efficient datapath (logical effort) logic
  - ♦ Example: rendezvous or *c-element*
    - Set function:  $\overline{ab} \mapsto o \uparrow$
    - Reset function:  $ab \mapsto o \downarrow$
    - What happens in states  $\notin \text{set} \cup \text{reset}$  ???

## Dynamic Logic

- *Transition* logic
- Specifies *set* and *reset* transitions
- Static states not explicitly specified or optimized
- Efficient datapath (logical effort) logic
  - ♦ Example: rendezvous or *c-element*
    - Set function:  $\overline{ab} \mapsto o \uparrow$
    - Reset function:  $ab \mapsto o \downarrow$
    - What happens in states  $\notin \text{set} \cup \text{reset}$  ???  
Output is FLOATING!

## Combinational Logic

- Function is fully specified by inputs
- Our most common design style
  - ♦ Example:  $f = a + b + c$

		ab			
		00	01	11	10
c	0	0	1	1	1
	1	1	1	1	1

## Sequential Logic

- Current state depends on previous state
  - ♦ Example: truth table for inverting c-element:

inputs	output
00	1
01	q
10	q
11	0

- Circuits typically contain **feedback**
- **Timing** may be critical to correct behavior
- Typical design mode for **asynchronous** circuits
  - ♦ why?

## Sequential Logic

- Current state depends on previous state
  - ♦ Example: truth table for inverting c-element:

inputs	output
00	1
01	q
10	q
11	0


- Circuits typically contain **feedback**
- **Timing** may be critical to correct behavior
- Typical design mode for **asynchronous** circuits
  - ♦ why? Async implements sequential state machines

## Sequential Logic

- How do you implement sequential logic with combinational gates?

 
## Sequential Logic

- How do you implement sequential logic with combinational gates?
- Feedback



 
## Sequential Logic

- How do you implement sequential logic with combinational gates?
- Feedback
- How do you implement sequential logic with dynamic gates?


 
## Sequential Logic

- How do you implement sequential logic with combinational gates?
- Feedback
- How do you implement sequential logic with dynamic gates?
- You can get it for free!
- Dynamic gates are naturally sequential



## Logic Circuit Styles

- The following will be discussed:
  1. Static combinational logic
  2. Pass transistor logic
  3. Dynamic logic
  4. Self-timed and asynchronous logic
  5. Self-resetting (pulse) logic

## Static Combinational Logic

- Used in **every** design!
- Main workhorse of our chips
- All commercial libraries have these cells
- Direct support based on CBD (cell based design), P&R, ...


## Key Circuit Effects

- Static Logic has good characteristics for key effects:
  - Reasonable power consumption (reactive, activity factors)
  - Simple & direct synthesis
  - High noise immunity
  - Timing validation (most common model)
  - Tolerant to process variation (time independent)
  - Tolerant to minor defects (high resistive bridging faults)
  - Scalable (shrinkable) to different process nodes
  - Testability (stuck at models, fault propagation, etc.)


 
## Transfer Function

- Useful for performance and noise characterization
  - Switch-point is location on transfer function where  $V_{out} = V_{in}$
  - Unity Gain Points determine signal attenuation and amplification voltages
- What happens to performance and noise when we skew SWP and UGP locations?



## Performance and Noise Metrics


- Electrical gain
  - FO-4 delay
  - Logical effort:  $f = gh \approx 4$
  - Too high – slow operation
  - Too low – wasted power and area
- Beta ratio, or gate skew
  - Balancing pullup/down currents:
    - equal rise/fall times
    - switch point at  $V_{DD}/2$
    - improved noise immunity
  - Skewed sizing:
    - improved performance in one direction

## Additional Important Circuit Effects

- These are also important to consider for all logic families
  - Transfer function
  - Delay variability
  - Switching thresholds
  - Body effect and sensitivity to signal ordering
  - Miller effect
  - Glitching
  - Crossover current

 
## Transfer Function

- Useful for performance and noise characterization
  - switch-point is location on transfer function where  $V_{out} = V_{in}$
  - Unity Gain Points determine signal attenuation and amplification voltages
- What happens to performance and noise when we skew SWP and UGP? *Response design dependent (can be worse!)*



## Gate Design Quiz

Following are a couple of gates:

 


Are these static or dynamic implementations?

What is the logic function of the above gates?

*Hint: The function is the same for both.*

 
## Ratioed NORs

- “Ratioed NOR” gates are much faster than static NORs
- These gates have relatively high crossover current in some states (which)?
- How do you size this device?
- What are the noise properties?



 
## Ratioed NORs

- “Ratioed NOR” gates are much faster than static NORs
- These gates have relatively high crossover current in some states (which)? when inputs not equal (1,0 or 0,1)
- How do you size this device?
- What are the noise properties?



 
## Ratioed NORs

- “Ratioed NOR” gates are much faster than static NORs
- These gates have relatively high crossover current in some states (which)? when inputs not equal (1,0 or 0,1)
- How do you size this device? weak p to n ratio
- What are the noise properties?


 
## Ratioed NORs

- “Ratioed NOR” gates are much faster than static NORs
- These gates have relatively high crossover current in some states (which)? when inputs not equal (1,0 or 0,1)
- How do you size this device? weak p to n ratio
- What are the noise properties? output may not be gnd



## Gate Delay Variability


- Internal parasitic values
- Signal switching order
- Multiple input switching
- MCF (Maximum capacitive Coupling Factor)
- Fanout load on gates
  - With inversion channel, effective  $t_{ox}$  increases, decreasing cap from gate to substrate
    - This gives different gate cap based on the logic state of the gate, and results in a varying capacitance as a gate switches!!!
- Body effect

## Glitching and Power

- **Activity factor** has direct effect on energy
  - Idle circuit only consumes leakage power  $P_{off} = W_{tot}V_{dd}I_{off}$
- Combinational logic is *reactive*
- Transient glitches propagate
- Approximately 15% of the power is due to *dynamic hazards*
 
## Crossover or Crowbar Current

- Current rushing between power and ground as p- and n-type devices are both on
- Dependent on slew rate of input signal
- Dependent on threshold of gate
- Consumes approximately 10% of the power in static gates with proper slopes



## Classifications of Static Gates

- Two flavors:
  - ◆ Simple
    - logical: single minterm
    - structural: no internal branching
  - ◆ Complex
    - logical: SOP format with multiple minterms
    - structural: *combination of multiple simple gates*

## Complex vs Simple Gate Design

- Classical design optimization problem:
  - ◆ Where is optimal benefit derived from jointly optimizing or partitioning logic functions or blocks?
  - ◆ What characteristics can be exploited or avoided?
  - ◆ What is local minima?
- Q: How does scaling effect our optimal choices?

## Complex vs Simple Gate Design

- Classical design optimization problem:
  - ◆ Where is optimal benefit derived from jointly optimizing or partitioning logic functions or blocks?
  - ◆ What characteristics can be exploited or avoided?
  - ◆ What is local minima?
- Q: How does scaling effect our optimal choices?  
Reduces the number of series transistors to output

## Simple Static Gate Design


- SOP minterm:  $\bar{f} = abc$ 
  - ◆ AND function
  - ◆  $\rightarrow$  n-type transistors in series
- POS minterm:  $\bar{f} = a + b + c$ 
  - ◆ OR function
  - ◆  $\rightarrow$  n-type transistors in parallel
- Note gates are naturally *inverting*
- Apply negative function directly to n-type devices
- Apply logical or structural duality transformation for p-types

## Simple Static Gate Design

- Example:  $\bar{f} = abc$
- Structural Algorithm
  1. Map minterm to n-type device
  2. P-types are structural dual of n-type tree
    - ◆ Series devices are in parallel
    - ◆ Parallel devices are in series
- Logical Algorithm
  1. Map minterm to n-type device
  2. Apply DeMorgan's theorem to minterm
  3. Implement p-type tree from derived equation
 
## Simple Static Gate Design

- $\bar{f} = abc$
- Show structural and logical derivations



## Structural Complex Static Gate Design


- Structural Derivation Algorithm 1
  1. Create p-type and n-type trees for all minterms
  2. Combine p-type and n-type minterms in series (SOP) or parallel (POS)
  3. Optimize network by sharing common transistors
- Structural Derivation Algorithm 2
  1. Create n-type (p-type) trees for all minterms
  2. Combine n-type (p-type) minterms in series (SOP) or parallel (POS)
  3. Optimize network by sharing common transistors
  4. Structurally take the dual of the network for the p-type (n-type) tree

## Logical Complex Static Gate Design

- Logical Derivation Algorithm
  1. Create minimized n-type pulldown logical representation using associative and distributive laws
  2. Map logic directly to n-type structure
  3. Apply DeMorgan's theorem to function
  4. Create minimized p-type pullup logical representation using associative and distributive laws
  5. Map logic directly to p-type structure

## Complex Static Gate Design

 - Example:  $\bar{f} = ac + ad + bc + bd$



## Logic Circuit Styles

- The following will be discussed:
  1. Static combinational logic
  2. **Pass transistor logic**
  3. Dynamic logic
  4. Self-timed and asynchronous logic
  5. Self-resetting (pulse) logic

## Pass Transistor Logic

- Used in *almost* every design
  - ♦ DRAM and SRAM cells
- Fine example of understanding capabilities and application needs
- Applied in other ways as well:
  - ♦ ALUs
  - ♦ Muxing
  - ♦ Interconnect
  - ♦ ...

## Pass Transistor Design

- Single-ended
  - ♦ Only pull-down function
- Differential
  - ♦ Pulldown function with dual
  - ♦ Both trees implemented in n-FET
  - ♦ *Sense amp* required for differential sensing
- Optimization point favors high complexity over simple functions

## Pass Transistor Logic Characteristics

- Potential significant performance advantage
- Linear resistive delay
- Can admit very complex functions in single DCN
- Pull up and down through same source transistor network
- Best differential performance with reset voltage between power rails

## Pass Transistor Logic Characteristics

- Can use *sense amp* (SA) for improved performance
  - ♦ Static power draw when active
    - Pulsed clocking
  - ♦ Limited active range
    - Normally skewed low
      - n-type logic
      - low voltage or ground as common reset reference

## Pass Transistor Logic Characteristics

- High sensitivity to noise:
  - ♦ Highly sensitive to differential noise
  - ♦ **Common mode** noise rejection
- Interfacing issues if not using SA
  - ♦ High voltage level restoration
  - ♦ Limited fan-in and fanout loads
  - ♦ Body effect

## Complementary Pass-Gate Logic

- Fast, common style for Function block pass logic
- Three varieties:
  1. Standard (p-type in driver not shut off)
  2. Keepers (dynamic logic inspired)
  3. Cross coupled (SA integration)

 


Figure 7.5 Complementary pass-gate logic implementations of XOR: standard CPL (a); cross-coupled CPL (b) [6].

## Complementary Pass-Gate Logic

- Clear difference in plots between standard and SA inspired
  - ♦ Full voltage generation
  - ♦ Reduced performance due to extra capacitance
- **Low threshold** transistor options for pass-gates
  - ♦ Noise and leakage ramifications

 


Figure 7.6 CPL operation of circuits shown in Fig. 7.5; external (a) and internal (b) node behavior [6].

11 → 01 transition on XOR



## LEAP Logic

- Random logic library, bidirectional cells
- Full functional block synthesis
- Single-ended methodology, "full" swing outputs
- Keeper to shut off p-FET in inverter
- Multiplexor based synthesis idea

 


Figure 7.7 LEAP pass-gate logic of NAND function [6].


## LVS Case Study: Double Pumped ALUs

Intel Pentium® 4 2× frequency low voltage swing integer core:<sup>1</sup>


- Performance benefit from halving the latency of integer operations
  - Reduce wait and impact of instruction dependencies
  - Improved bypass operations
  - Store to load forwarding mechanism
- Greater complexity than entire Pentium Pro® design (6.8 million non-array transistors)
- Pulsed clocks

<sup>1</sup>US Patent 6,557,149: Algorithm for finding vectors to stimulate all paths and arcs through an LVS gate", Morriss & Stevens.

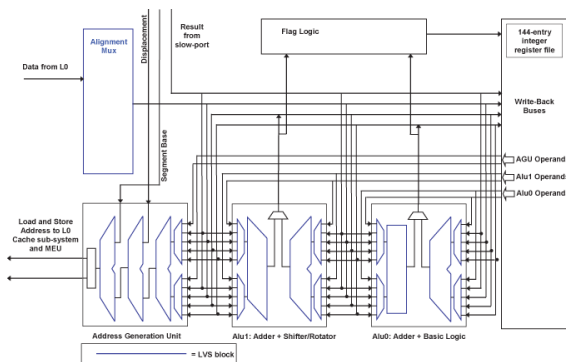
## Low Voltage Swing Logic Bypass Architecture





## Low Voltage Swing Core

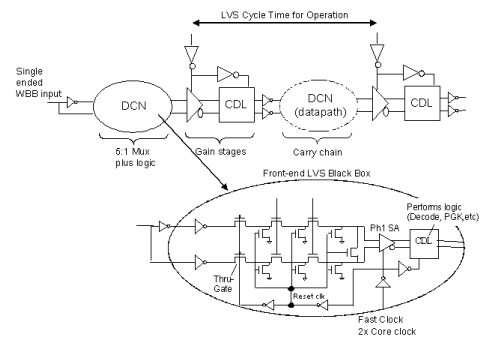


## Manchester Carry Chain

 


## Low Voltage Swing Adder

  

LVS XOR CELL

 


LVS PGK CELL

 



LVS SKIP CELL

## Sense Amp and Drive Gain

 

## Low Voltage Swing Validation

  1. 6.8 GHz in 3.4 GHz product
2. 6 transistor stages in 2 FO4 delays
3. Pulse clock
4. Complex path calculation
5. Common mode noise



## Logic Circuit Styles

- The following will be discussed:
  1. Static combinational logic
  2. Pass transistor logic
  3. **Dynamic logic**
  4. Self-timed and asynchronous logic
  5. Self-resetting (pulse) logic

## Dynamic Logic

- *Transition* logic
- Specifies *set* and *reset* transitions
- Static states not explicitly specified or optimized
- Efficient datapath (logical effort) logic
  - ♦ Example: rendezvous or *c-element*
    - Set function:  $\overline{a}\overline{b} \mapsto o \uparrow$
    - Reset function:  $ab \mapsto o \downarrow$
    - What happens in states  $\notin \text{set} \cup \text{reset}$  ???

## Dynamic Logic

- *Transition* logic
  - Specifies *set* and *reset* transitions
  - Static states not explicitly specified or optimized
  - Efficient datapath (logical effort) logic
    - ♦ Example: rendezvous or *c-element*
      - Set function:  $\overline{a}\overline{b} \mapsto o \uparrow$
      - Reset function:  $ab \mapsto o \downarrow$
      - What happens in states  $\notin \text{set} \cup \text{reset}$  ???
- Output is tristated

## Dynamic Logic Characteristics

- Monotonic functions
  - ♦ Due to dynamic state, glitching inputs can be fatal
- Cannot assert both set and reset functions
  - ♦ Automatically controlled with "footed" logic. ("footed" will be defined)


## Dynamic Logic

- **Domino logic** is most common form of dynamic logic
- Used in two forms:
  1. Precharge logic
    - a. clocked precharge logic
    - b. self-resetting logic
  2. Set reset functions

## Domino Logic


- Optimizes the pullup (p-FET) trees:
  - ♦ *Only a single p-type pullup!*
- Allows complex pulldown function.
- Two classes
  - ♦ Footed
    - The pullup signal is ANDed with pulldown function
  - ♦ Unfooted
    - The pullup signal does not exist in the pulldown function

## Domino Logic

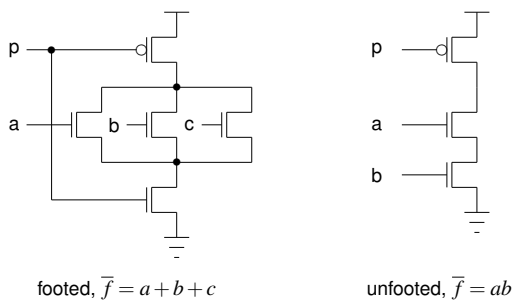

- Do we want footer at top or bottom of stack? Why?

## Domino Logic

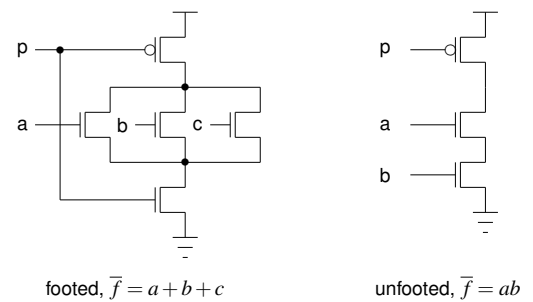

- Do we want footer at top or bottom of stack? Why?  
Bottom, to minimize parasitics and body effect.

## Domino Advantage

Can you have a gate with a logical effort less than one?

## Domino Advantage

- Low data input load to output drive ratios (*gain*)

Gate	Static	Domino	Prech
2-NAND, unfooted	4/3	2/3	2/3
2-NAND, footed	4/3	3/3	5/3
3-NAND, unfooted	5/3	3/3	2/3
3-NAND, footed	5/3	4/3	6/3
2-NOR, unfooted	5/7	1/3	2/3
3-NOR, unfooted	7/3	1/3	2/3
3-NOR, footed	7/3	2/3	4/3

- What about logical effort of complex pulldown functions?

## Domino Advantage


- Low data input load to output drive ratios (*gain*)

Gate	Static	Domino	Prech
2-NAND, unfooted	4/3	2/3	2/3
2-NAND, footed	4/3	3/3	5/3
3-NAND, unfooted	5/3	3/3	2/3
3-NAND, footed	5/3	4/3	6/3
2-NOR, unfooted	5/7	1/3	2/3
3-NOR, unfooted	7/3	1/3	2/3
3-NOR, footed	7/3	2/3	4/3

- What about logical effort of complex pulldown functions?  
Also MUCH improved!!!
 
## Dynamic Gate Noise

- **Keepers** can be used to mitigate this somewhat
  - Size of keeper limited by relation to set/reset stack strength
  - Nominally used to combat leakage current
  - Increases crowbar current of gate as it fights almost the whole transition.



## Keepers

- Jam-latch keepers are  $W$  ratioed to approximately 5–20% of reset tree.
- Should feedback inverter be in the output path?  
NO, due to:
  - Coupling control
  - Latency
- Do we need to use both a p- and n-type keeper FET?

## Domino Disadvantages

- Only three main disadvantages:
  - Noise, noise, and noise
    - Due to: coupling, parasitic charge sharing, leakage
- Other argued disadvantages...
  - Energy consumption
    - Precharge activity factor (clocked modes)
  - Additional timing requirements

## Keepers


- Jam-latch keepers are  $W$  ratioed to approximately 5–20% of reset tree.
- Should feedback inverter be in the output path?

## Keepers

- Jam-latch keepers are  $W$  ratioed to approximately 5–20% of reset tree.
- Should feedback inverter be in the output path?  
NO, due to:
  - Coupling control
  - Latency
- Do we need to use both a p- and n-type keeper FET?  
Depends
  - Usage of gate (precharge or set/reset)
  - N-type removed for many precharge logics.

 
## Dynamic Gate Noise

- **Keepers** can be used to mitigate this somewhat
  - ♦ Size of keeper limited by relation to set/reset stack strength
  - ♦ Nominally used to combat leakage current
  - ♦ Increases crowbar current of gate as it fights almost the whole transition.


 
## Domino Advantage

Go figure - there actually *can* be a noise advantage with domino.



From research by Santhanam & Stevens on *Complementary Dynamic Logic*. (Related to Noise Tolerant Precharge NTP)

## Clocked (Precharge) Domino Implications

- Clock connected to precharge
- Each domino input is low at start of evaluate phase
- Clock allows synchronization and latching
- Disadvantages
  - ♦ *Power*: precharge occurs independent of data activity factor
  - ♦ *Performance*: footed implementation adds series device
  - ♦ *Performance*: unbalanced evaluate and precharge phases
    - Evaluate dependent on logic depth
    - Concurrent precharge in constant time (two gate delays)
  - ♦ *CAD*: more difficulty to synthesize, place & route, etc.

## Clocked (Precharge) Domino Configuration

- Alternate domino and static gates
- Optimize evaluation path
  - ♦ Always evaluate data pulldown in domino
  - ♦ Always evaluate data pullup in static
  - ♦ Therefore, skew logic:
    - Up to a factor of 6/1 sizing skew
    - Skew both static and domino
    - ... but this decreases noise margins!
  - ♦ Therefore, very simple static gates


## Timing for Precharge Domino

1. Precharge pulse sufficient to charge outputs
2. Falling input transitions require positive setup before precharge ends
3. Rising edge setup sufficient to discharge & latch output
4. Rising inputs require hold time to fully drive output

## Clocked Unfooted Domino

- First stage normally footed
- Internal stages can be unfooted
  - ♦ Crowbar current serious reliability, power, noise issue
  - ♦ Avoid by delayed clock
    - Precharge clock delay  $\geq$  logic precharge
    - Logic precharge skewed slow?
    - Symmetric delay effects evaluation delay

## Clocked Unfooted Domino

 

## Dynamic Noise Sources

- Leakage current can be substantial in wide OR structures
- Charge sharing
  - precharge internal nodes
- Interconnect coupling
- Ground bounce

## Dynamic Noise Sources


- **Dynamic Carrier Noise Injection**
  - Nodes driven below ground and above  $V_{DD}$
  - Forward biases diodes
  - Injects minority carriers into substrate and well
- Collected by nearby diffusion
- Particularly onerous near pads and clock drivers
  - Pads always use “guard ring” for this purpose
- Effect reduces with voltage scaling due to diode forward bias threshold

## Area & Leakage

- Dynamic logic uses less area than static:
  - PMOS tree replaced with single FET
  - NMOS tree can combine multiple gates
- Translates to substantially lower  $W_{tot}$  (leakage)


## Dynamic Noise Sources

- **Miller and Backgate Coupling**

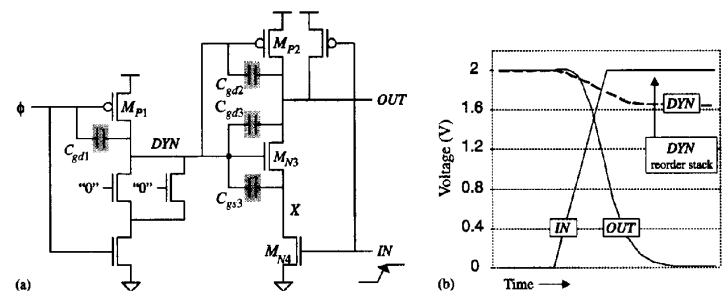


**Figure 8.13** Back-gate coupling: (a) circuit diagram; (b) signal waveforms.
 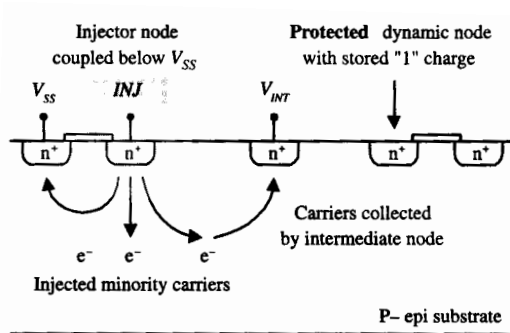
## Dynamic Carrier Noise Injection




## Dynamic Carrier Protection



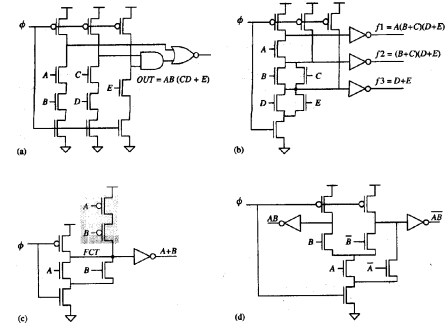
## Other Domino Forms

- Compound Domino, Multiple-output domino, noise-tolerant precharge (NTP), dual-rail domino




## Other Dynamic Structures

- NORA Logic

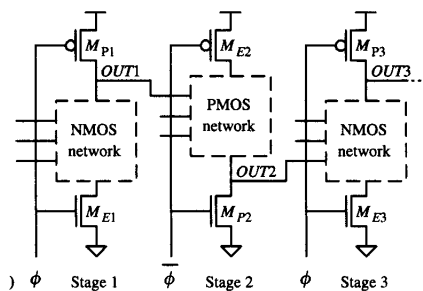


## Other Dynamic Logic

- DRAM
- Dynamic Latches:

 

## Dual Rail Domino

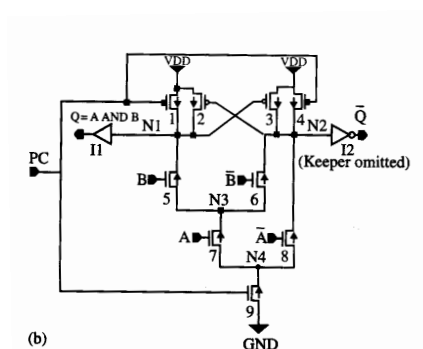

## DCVS

- A combination of pass-gate logic and Domino
- True dual-rail domino
- Sense-Amp inspired

 


Figure 7.4 Basic DCVSL AND gate with PMOS cross-coupled loads [6].

## Logic Circuit Styles

- The following will be discussed:
  1. Static combinational logic
  2. Pass transistor logic
  3. Dynamic logic
  4. **Self-timed and asynchronous logic**
  5. Self-resetting (pulse) logic

## Set Reset Domino


- Normally applied in Asynchronous Logic
  - Maps very well to sequential protocols
- Resolves clocked dynamic problems:
  - Not precharged
    - No phases - dependent on set/reset transition delays
    - Data activity factor  $\propto$  active power
  - Sequential asynchronous synthesis quite mature

## Asynchronous Domino Example

- Sequential circuit design natural for domino gates
- Ultra low power and high gain sequential design
  - Both active and leakage energy
  - Activity factor dictates active energy
  - No glitching
- Not required to have static gate between dominos
  - Based on transitions and logic levels

 
## Asynchronous Domino Example

Asynchronous Pentium instruction length decoder branch control circuitry




## Asynchronous Domino Example

High performance pipeline controller

 


## Domino FIFO controller

 



 
## Non-Domino Precharge

- C-element
- Generalized C-element
  - ◆ Complicated multiple PMOS structure
  - ◆ Slower than domino
  - ◆ Hazard removal, reduced timing constraints


 
## Static Asynchronous Logic

- Can implement with static gates
- Generally worse than with dynamic gates
  - ◆ slower
  - ◆ higher power
  - ◆ larger area



## Logic Circuit Styles


- The following will be discussed:
  1. Static combinational logic
  2. Pass transistor logic
  3. Dynamic logic
  4. Self-timed and asynchronous logic
  5. **Self-resetting (pulse) logic**

## Self-Resetting Domino


- Pulse-logic
- Combination between precharge and set/reset design
  - ◆ Self-precharged after each evaluation
  - ◆ Only precharges if data is set
    - allows energy  $\propto$  activity factors
- Challenging design issues:
  - ◆ Pulse-width
  - ◆ Pulse filtering
  - ◆ Pulse ANDing

## Intel “Self-Terminating Precharge”

### Double Pumped ALU

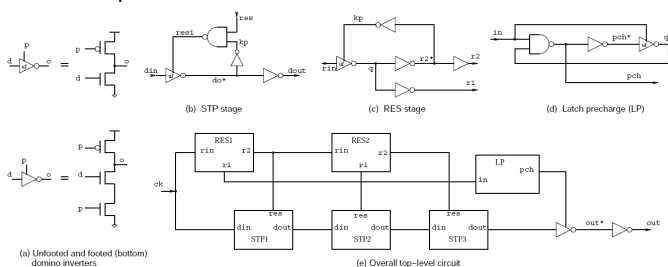

## Asynchronous GasP

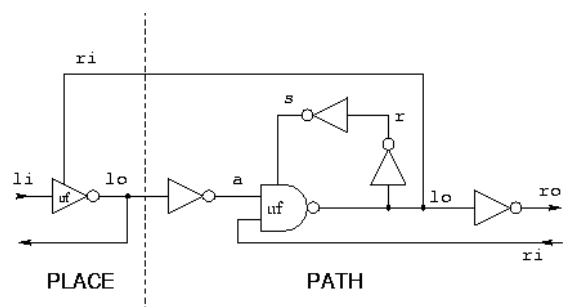

### Logic Circuit Styles Review

- key metrics for choosing logic design style
- difference between static and dynamic logic
- combinational vs sequential logic
- static logic characteristics
- circuit skewing
- ratioed gates
- sources of gate variability
- MCF

### Logic Circuit Styles Review

- signal switching order
- fanout loads
- activity factor's effect on circuit power
- glitching
- crowbar current
- simple and complex gate transistor optimization
- static logic optimization point
- common pass transistor logic applications

### Logic Circuit Styles Review

- single vs differential pass gate design
- pass gate optimization point
- sense amp
- pass gate noise: common mode
- threshold effect on pass gate logic
- monotonic nature of dynamic logic
- characteristics of domino logic
- footed vs unfooted domino

### Logic Circuit Styles Review

- primary domino advantage and disadvantage
- keepers, ratio, p vs n-FET
- precharge domino configuration, disadvantages, skews, ...
- dynamic logic noise source
- dynamic carrier noise injection
- async domino characteristics
- async domino advantages
- self-reset domino advantages and challenges

### Review

- Compare logic styles in terms of:
  - ♦ gate capacitance (logical effort)
  - ♦ complementary p-type trees and their effect on power & performance
  - ♦ power (due to reactive nature of logic (activity factors))
  - ♦ glitching, crowbar power, voltage level restoration, etc.