

The unknown component problem

①

Given specification polynomial $f \in \mathbb{F}_q[x_1, \dots, x_n] = \mathbb{R}$
 $q = 2^K$, and a ckt C with 'S' gates.

Write the gates as polynomials in \mathbb{R} as


$$F_i = \{f_1, \dots, f_i, \dots, f_s\}, \quad J = \langle f_1, \dots, f_i, \dots, f_s \rangle$$

Assume the circuit C correctly implements f .

$$\text{Then } f \in \mathcal{I}(\mathbb{F}_q(J)) = J + J_0 \quad (J_0 = \langle x_i^q - x_i \rangle)$$

Assume $J \supset J_0$.
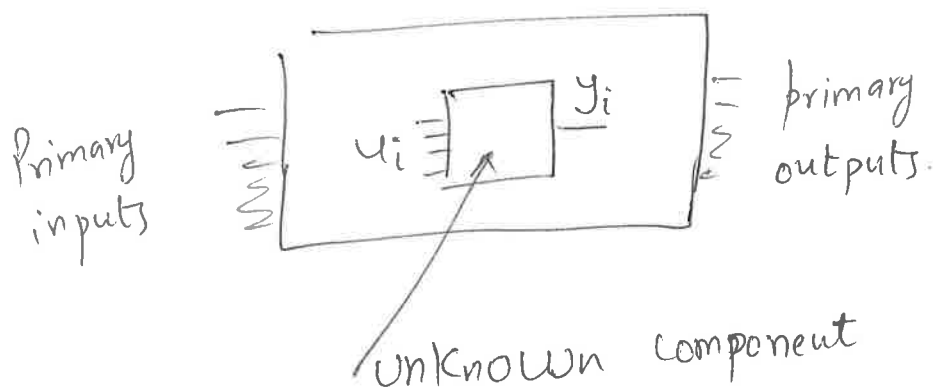
$$\text{So } f \in J \Rightarrow f = h_1 f_1 + \dots + h_i f_i + \dots + h_s f_s$$



$$f_i = y_i + P_i(u_i)$$

$y_i > u_i$ in our term order.

$$h_i f_i = f + h_1 f_1 + \dots + h_{i-1} f_{i-1} + h_{i+1} f_{i+1} + \dots + h_s f_s$$

$$\text{or } h_i f_i \in \underbrace{\langle f, f_1, \dots, f_{i-1}, f_{i+1}, \dots, f_s \rangle}_{\text{ideal } J'}$$

(2)

Now $f_i = y_i + \underbrace{P(u_i)}$

↳ some polynomial in u_i

but $h_i \in R$ is arbitrary.

Our question was, what if we project the variety of J' on y_i & u_i coordinates?
Can we recover f_i ?

Is $h_i f_i \in J' \cap F_q[y_i, u_i]$?


Yes, but that does not always help us recover f_i . Sometimes it does, but not always.

Here is an example that shows that some information is missing.

See Fig 1.

Specification $f = z + ac + a + b + bc + c$

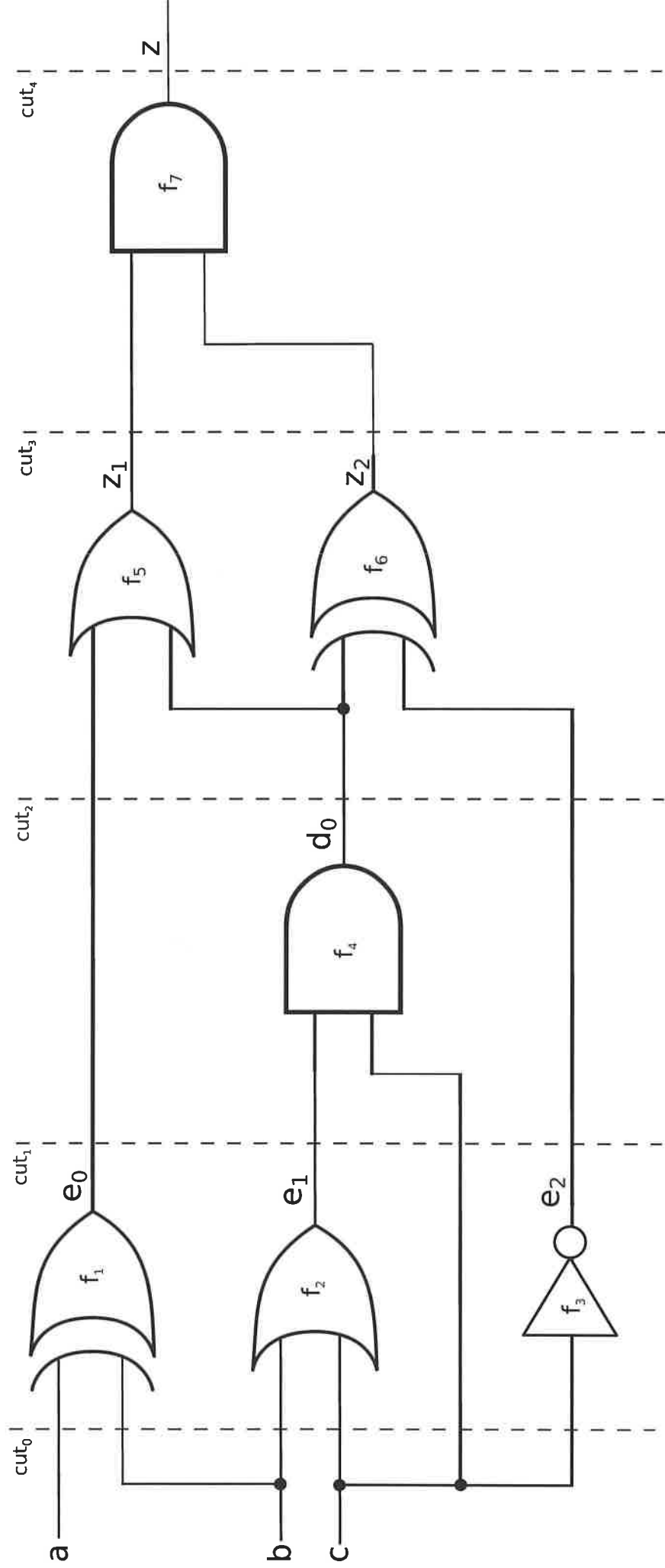Ring $f_2 [z, z_1, z_2, e_0, e_2, a, b, d_0, e_1, c]$



Assume f_4 $d_0 = e_1 \wedge c$ is the unknown component.
 $[d_0 + e_1 \cdot c \text{ in } \mathbb{F}_2]$

Fig 1.

Polynomials of this ckt

$$f_1: e_0 + a + b$$

$$f_2: e_1 + bc + b + c$$

$$f_3: e_2 + c + 1$$

$$f_4: d_0 + e_1 \cdot c \text{ [unknown gate]}$$

$$f_5: z_1 + e_0 d_0 + e_0 + d_0$$

$$f_6: z_2 + d_0 e_2$$

$$f_7: z_0 + z_1 \cdot z_2$$

$$+ \overline{z_0}.$$

(5)

$$f \in \langle f_1, f_2, \underline{f_4}, f_7 \rangle$$

\downarrow
Unknown.

$$\text{Let } f_4 = \underline{d_0 + P(e_1, c)}$$

what is P ?

Notice the function implemented by f_4 .

e_1	c	\rightarrow	d_0		
0	0		0	}	$d_0 = \text{AND}(e_1, c).$ $P(e_1, c) = \underline{\underline{e_1 \cdot c}}$
0	1		0		
1	0		0		
1	1		1		

$$h_4 f_4 \in \langle f, f_1, \dots, f_3, \underline{f_5}, \dots, f_7 \rangle$$

$\underbrace{\hspace{10em}}_{J'}$

Compute reduced Gröbner Basis of

$$J_L = J' \cap \mathbb{F}_2[d_0, e_1, c]$$

J_L = elimination ideal that eliminates everything but d_0, e_1, c .

$$GB(J_L + J_0) = G = \{g_1, g_2, \dots, g_5\}$$

(6)

$$= g_1: c^2 + c$$

$$g_2: e_1 c + c$$

$$g_3: e_1^2 + e_1$$

$$g_4: d_0 c + c$$

$$g_5: d_0^2 + d_0$$

$$V(G) = \begin{array}{c} \checkmark \\ \checkmark \\ \checkmark \\ \checkmark \end{array} \begin{array}{ccc} e_1 & c & d_0 \\ 0 & 0 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \\ 1 & 0 & 1 \\ 1 & 1 & 1 \end{array}$$

$\checkmark = \text{pts in } V(f_4)$

Recall $h_4 f_4 \in J' \quad (J' \supset J_0)$

$V(h_4 f_4) \supset V(J')$. Now project variety on e_1, c, d_0 .

Projection is also a variety

So $V(h_4 f_4)|_{e_1, c, d_0} \supset V(J_L + J_0)$

$$\boxed{V(h_4) \cup V(f_4) \supset V(J_L + J_0)} \quad (1)$$

(7)

Notice the point $e, c, d_0 = (010) \in V(f_4)$
but is not in $V(J_L + J_0)$.

From this information, do you think
 $V(f_4)$ can be found?

Notice $f_4 = d_0 + P(e, c)$

$\exists h_4$ s.t. $h_4 \cdot f_4 \in J_L + J_0$.

If $h_4 = c$, then

$$c \cdot [d_0 + P(e, c)] = \underbrace{g_2 + g_4}_{\in G}$$

$$= \underline{e, c + d_0 c}$$

then $P(e, c) = e, c$

but how do we guess h_4 ?
