 


## Where are we?


- ▶ Lots of Layout issues
  - ▶ Line of diffusion style
  - ▶ Power pitch
  - ▶ Bit-slice pitch
  - ▶ Routing strategies
  - ▶ Transistor sizing
  - ▶ Wire sizing

## Layout - Line of Diffusion

- ▶ Very common layout method
  - ▶ Start with a "line of diffusion" for each transistor type
  - ▶ Cross with poly to make transistors
  - ▶ This is the "type 2" NOR gate




## Line of Diffusion in General

 


- ▶ Start with lines of diffusion for each transistor type

## Line of Diffusion in General

 

- ▶ Cross with Poly to make transistors


## Line of Diffusion in General

 

- ▶ Now break and connect diffusion
  - ▶ There's our NOR gate
 
## Stick Diagrams

- ▶ You can plan things with paper and pencil using Stick Diagrams
  - ▶ You'll need colored pencils
  - ▶ Draw lines for layers instead of rectangles
  - ▶ Then you can translate to layout



[illegible]

# Gate Layout

- ▶ Layout can be very time consuming
  - ▶ Design gates to fit together nicely
  - ▶ Build a library of standard cells
- ▶ Standard cell design methodology
  - ▶  $V_{DD}$  and GND should abut (standard height)
  - ▶ Adjacent gates should satisfy design rules
  - ▶ nMOS at bottom and pMOS at top
  - ▶ All gates include well and substrate contacts

# Example: Inverter

(a)

(b)

Well Tap


V<sub>DD</sub>

GND

A


Y


Substrate T

 

## Example: NAND3

- ▶ Horizontal N-diffusion and P-diffusion strips
- ▶ Vertical polysilicon gates
- ▶ Metal1  $V_{DD}$  rail at top
- ▶ Metal1 GND rail at bottom
- ▶  $32\lambda$  by  $40\lambda$
- ▶  $9.6\mu \times 12\mu$
- ▶  $-\lambda = .3\mu$

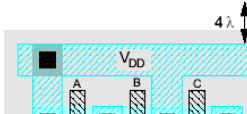- ▶ Horizontal N-diffusion and P-diffusion strips
  - ▶ Vertical polysilicon gates
  - ▶ Metal1  $V_{DD}$  rail at top
  - ▶ Metal1 GND rail at bottom
  - ▶  $32\lambda$  by  $40\lambda$
  - ▶  $9.6\mu \times 12\mu$
  - ▶  $-\lambda = .3\mu$
- 
- The diagram shows a cross-section of a device. At the top is a cyan hatched layer labeled  $V_{DD}$ . Below it is a grey layer. In the center, there are three vertical structures labeled A, B, and C. Structure A is a grey vertical strip. Structure B is a grey vertical strip with a cyan hatched gate on top. Structure C is a grey vertical strip with a cyan hatched gate on top. To the right of these structures is a cyan hatched region labeled  $V_{DD}$ . At the bottom is a grey layer. A vertical double-headed arrow on the right indicates a height of  $4\lambda$ . The structures A, B, and C are connected to a horizontal grey strip at the bottom. The cyan hatched regions are connected to a horizontal cyan hatched strip at the top.

 


# Stick Diagrams

- ▶ *Stick diagrams* help plan layout quickly
  - ▶ Need not be to scale
  - ▶ Draw with color pencils

Legend:

- Contact
- Metal1
- pdiff
- ndiff
- Polysilicon

 - ▶ *Stick diagrams* help plan layout quickly
  - ▶ Need not be to scale
  - ▶ Draw with color pencils



# Wiring Tracks

- ▶ A *wiring track* is the space required for a wire
  - ▶  $1.2\mu$  width,  $1.2\mu$  spacing from neighbor =  $2.4\mu$  pitch
- ▶ Transistors also consume one wiring track


In our rules minimum M1 and M2 width & spacing is  $3\lambda$ , so minimum pitch is  $1.8\mu$ ;  
Contact rule is larger!

(a)

(b)


- ▶ A *wiring track* is the space required for a wire
  - ▶ 1.2 $\mu$  width, 1.2 $\mu$  spacing from neighbor = 2.4 $\mu$  pitch
- ▶ Transistors also consume one wiring track

 In our rules minimum  
M1 and M2 width &  
spacing is  $3\lambda$ , so  
minimum pitch is  $1.8\mu$ ;  
Contact rule is larger!



 
## Well spacing

- Wells must surround transistors by  $1.8u$ 
  - Implies  $3.6u$  ( $12\lambda$ ) between opposite transistor flavors
  - Leaves room for one wire track


 
## Area Estimation

- Estimate area by counting wiring tracks
  - Multiply by 8 to express in  $\lambda$ , or by 2.4 to express in microns




## Example: O3AI

- Sketch a stick diagram for O3AI and estimate area
  - $Y = \overline{(A+B+C)} \cdot D$

 
## Example: O3AI

- Sketch a stick diagram for O3AI and estimate area
  - $Y = \overline{(A+B+C)} \cdot D$


 
## Example: O3AI


- Sketch a stick diagram for O3AI and estimate area
  - $Y = \overline{(A+B+C)} \cdot D$



## Euler Paths

- A graphical method for planning complex gate layout
  - Take the transistor netlist and draw it as a graph
  - Note that the pull-up and pull-down trees can be duals of each other
  - Find a path that traverses the graph with the same variable ordering for pull-up and pull-down graphs
  - This guides you to a line of diffusion layout


## Simple example: NOR

 

- ▶ Euler path is a tour of all edges
- ▶ Find a path that has the same ordering for pull-up and pull-down, i.e. **A B**
  - ▶ Vdd A 1 B Out
  - ▶ GND A Out B GND
 
## This Path Translates to Layout

- ▶ Find a path that has the same ordering for pull-up and pull-down, i.e. **A B**
  - ▶ You can also include all the internal nodes
  - ▶ Pull-up: **Vdd A 1 B Out**
  - ▶ Pull-Down: **GND A Out B GND**
  - ▶ Line of diffusion layout




## Examples

- ▶ Switch to chalkboard for examples
  - ▶ Hopefully with colored chalk...

 
## Layout Example: Flip Flop

- ▶ Simple D-type edge triggered flip flop



 
## Zoom in on Latch

- ▶ Need two copies of this for a full D flip flop



 
## Stick Diagram of Latch

- ▶ First add the gates
  - ▶ Note where outputs can be shared
  - ▶ Ignore details of signal crossings for now...



 
## Stick Diagram of Latch

- First add the gates
  - Note where outputs can be shared
  - Ignore details of signal crossings for now...



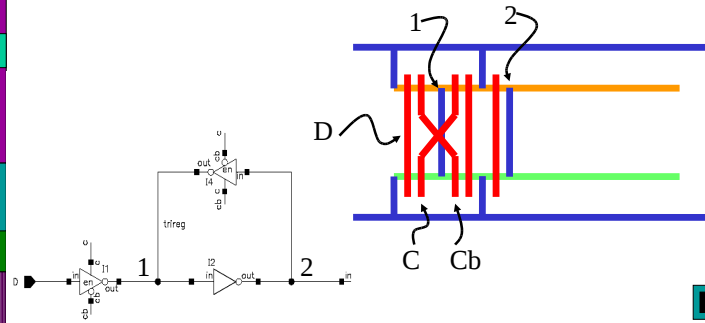
## Stick Diagram of Latch

- First add the gates
  - Note where the signals are relative to the schematic



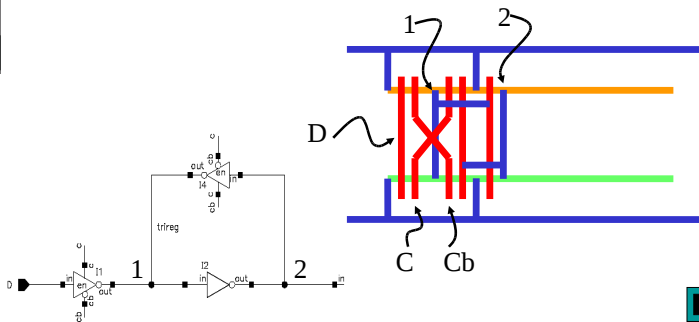
## Stick Diagram of Latch

- First add the gates
  - Note where the signals are relative to the schematic
  - Note where additional connections are needed



 
## Start With First Enabled Inv

- I'm using 5u power wires, 29u vertical pitch based on a C5x standard cell model from AMI
  - Probably overkill...
- Add DIF for N- and P-type transistors
  - Note 2x standard size because of serial connection



 
## Add Next Enabled Inverter

- Add two more poly gates for second enabled inverter
- Note that the two enabled inverters share an output (not connected yet)
- Note that I've added vdd! and gnd! For DRC
- I'll deal with C-Cb crossover later...





## Aside: Multiple Contacts

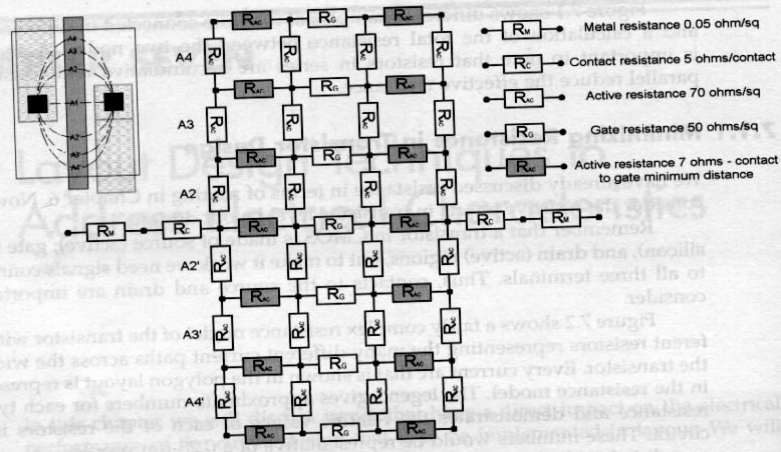

- Look at a model of transistor resistance





## Contact Option #1

  

▶ Total equivalent resistance = 56.1 Ohms

- ▶ Metal resistance = 0.05  $\Omega$ /square
- ▶ Contact resistance = 5  $\Omega$ /contact
- ▶ Active resistance = 70  $\Omega$ /square
- ▶ Gate resistance = 50  $\Omega$ /square
- ▶ Active resistance 70 - contact to gate



## Contact Option #2

  

Case 2

▶ Total equivalent resistance = 105.1 Ohms

## Contact Option #3

  


Case 3

- ▶ Total equivalent resistance = 24.7 Ohms
- ▶ So, put in as many contacts as will fit along side a wide gate...

 
## Meanwhile, Add inverter

- ▶ Note that it's back to standard size
- ▶ Shares vdd/gnd connection with enabled inverter
- ▶ Minimum spacing for all transistors so far
  - ▶ Incremental DRC at EVERY step!



 
## Finish Inverter (mostly)

- ▶ Make inverter output connections
  - ▶ Don't connect yet
  - ▶ I'm going to use M1 as a horizontal layer
  - ▶ Which means being careful about vertical use of M1




 
## Make Feedback Connections

- ▶ Output of inverter (connected in M1 for now) goes to input of 2<sup>nd</sup> enabled inverter
- ▶ Output of enabled inverters goes to input of inverter
  - ▶ Note that output of enabled inverters goes through POLY



  
## Deal With C/Cb Crossover

- Start by cutting the "select" gates of the enabled inverters



 
## Connect the C Input

- Prepare for M1 crossover in C wire
  - C is N-type in first enabled inverter, P-type in second enabled inverter
  - Use M1PLY contacts
- PROBLEM! We need to squeeze a poly wire inbetween those contacts...
  - Use design rules to plan for space



 
## Look at Gap

- You need to have enough space for minimum width poly to fit through gap



 
## Start Making Room

- Push D-signal poly out of the way with minimum spacing to DIF
  - We'll move it back later
- Make sure to continue to DRC at every step!



 
## Fit Things Back Together

- Jog the poly around and through the gap with minimum spacing to M1PLY contact on both sides



 - Now put big D-poly jog back as close as you can





 
## Plan For Clock Routing



- ▶ Add M1PLY contacts for future connections

- ▶ Need to get Cb, C, D signals into the latch in the future
- ▶ Those will most likely be routed on some type of metal
- ▶ So we need the M1 metal connection at the bottom




- ▶ Break M1 output connection on inverter to leave room for horizontal M1 routing

  - ▶ I'll eventually route C and Cb through the cell horizontally on M1



 
## Bit Slice Plan

- ▶ Plan is to stitch these together to make a register
  - ▶ Inputs on top in M2
  - ▶ Outputs on bottom in M2
  - ▶ Clock and Clock-bar routed horizontally in M1



 
## Need Second Latch

- ▶ Basically a copy of the first latch
  - ▶ But with reversed C and Cb connections
  - ▶ Copy the first layout...


 
## Expand from Latch to F/F


- ▶ Select and copy the first latch
- ▶ Now I need to reverse the C and Cb connections



## C/Cb Routing Plan

- ▶ Remember my C/Cb routing plan


- ▶ Plan for where those wires can go

 



 
## C/Cb Routing Plan

- Remember my C/Cb routing plan
- Plan for where those wires can go



 
## Connect Clocks to 1<sup>st</sup> Latch

- Adjust contact positions for the first enabled inverter



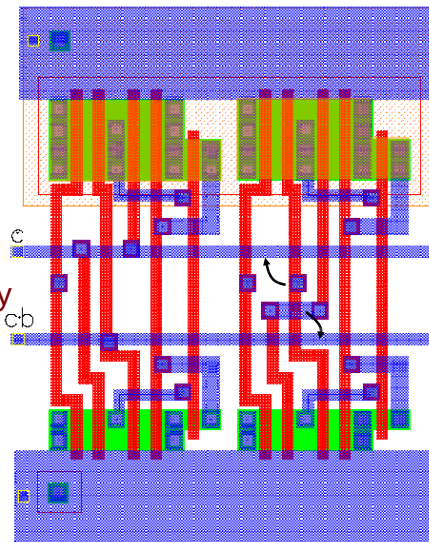
## Connect Clocks to 2<sup>nd</sup> Latch

- Now shift the contacts the other way for the second latch
- Makes the complementary C/Cb connection



 
## Connect Clocks to 2<sup>nd</sup> Latch

- Now shift the contacts the other way for the second latch
- Makes the complementary C/Cb connection



 
## Connect the Two Latches

- Q of first goes to D of second
- Don't really need both top and bottom connections, but it doesn't hurt
- Lower resistance paths


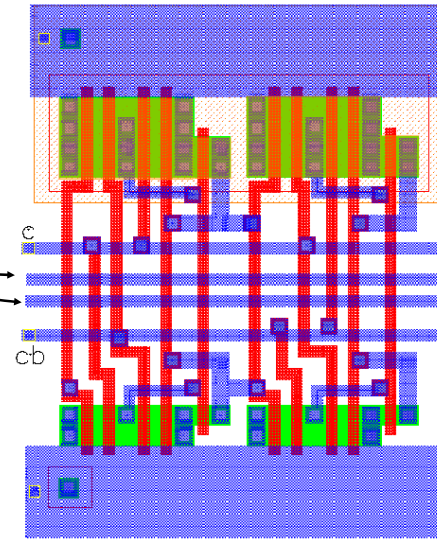
## Note Extra Routing Channels


- Note that this vertical pitch, and this cell contents have left two additional M1 horizontal routing channels through the middle of the cell




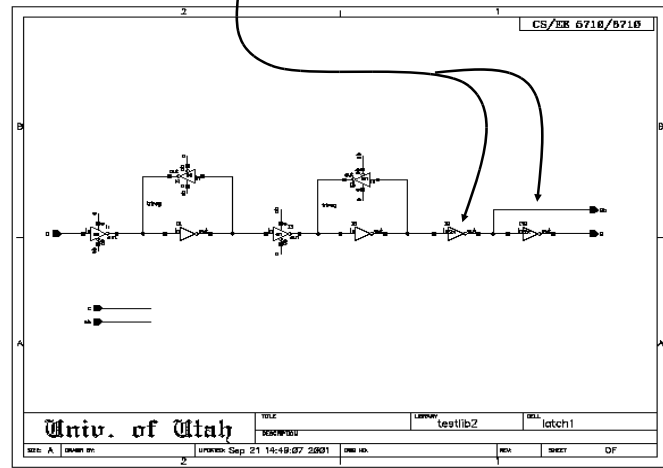
## Now Consider Output Inverters


- Two more inverters
- Make them 2x size for output drive



## Output Inverters


- Add the DIF for the output inverters

- Remember I want to make them 2x size

 

 
## Make Output Connections

- Add vdd, gnd and output contacts
- Add poly gates
- Make output connections in M2
- Connect to 2<sup>nd</sup> latch and to 2<sup>nd</sup> inverter



 
## Now Squeeze Inverter

- Select regions of the layout and stretch to move it all to a new spot




## Keep Squeezing

- Now squeeze power supply contacts

 

 
## Squeezed Version

- Output inverters squeezed together
- Note that D, Q, And Qb are routed vertically in M2



 
## Final D-Type Flip Flop

- ▶ Squeeze vertically since I don't need extra routing channels, and I don't need to match with standard cells
- ▶ Add long NWELL and SUB contacts




## Put Four of them Together

 

- ▶ Add instances that abut
  - ▶ Or use the "array" feature of the instance dialog
- ▶ Note that C and Cb are routed in horizontal M1

## Zoom in to Cell Boundary

 

- ▶ There's a little extra space
  - ▶ Caused by wanting each latch to DRC on its own
  - ▶ Could close this up by overlapping cells